

## AND Gate

2 min

Our next gate is the *AND gate*. This gate receives two inputs and only returns current if the inputs are both *on*.

As in previous exercises, you'll only be able to use gates you've previously built: `NAND_gate()`, and `NOT_gate()`.

Here's the truth table:

<i>a</i>	<i>b</i>	output
0	0	0
0	1	0
1	0	0
1	1	1

### Instructions

1. Checkpoint 1 Passed

#### 1.

Define `AND_gate()` which has two parameters `a` and `b`.

`AND_gate()` should return 1 if both `a` and `b` are 1. It should return 0 otherwise.

Hint

The first gate we built, `NAND_gate()` is short for NOT AND gate.

```
NAND_gate(1, 1)
```

```
# 0
```

```
NAND_gate(0, 1)
```

```
# 1
```

```
# meanwhile...
```

```
AND_gate(1, 1)
```

```
# 1
```

```
AND_gate(0, 1)
```

```
# 0
```

to Clipboard

In other words, AND is the **negated** version of NAND. We can "negate" an output with our previous gate:

```
NOT_gate(NAND_gate(1, 1)) == AND_gate(1, 1)
```

```
# True
```

**script.py**

```
from nand import NAND_gate  
from not_gate import NOT_gate
```

```
def AND_gate(a, b):
```

```
    if a and b:
```

```
        return 1
```

```
    else:
```

```
        return 0
```

```
# TEST CASES
```

```
print("A: 0, B: 0 | Output: {0}".format(AND_gate(0, 0)))
```

```
print("A: 0, B: 1 | Output: {0}".format(AND_gate(0, 1)))
```

```
print("A: 1, B: 0 | Output: {0}".format(AND_gate(1, 0)))
```

```
print("A: 1, B: 1 | Output: {0}".format(AND_gate(1, 1)))
```