

OR Gate

3 min

The next gate we are going to build is the *OR gate*. This gate receives two inputs and returns 1 if either one of the inputs is 1.

To build your `OR_gate()`, you should use any combination of the gates you've already made: `NAND_gate()`, `NOT_gate()`, and `AND_gate()`.

Here's the truth table:

a	b	output
0	0	0
0	1	1
1	0	1
1	1	1

Instructions

1. Checkpoint 1 Passed

1.

Define `OR_gate()` which takes two inputs, `a` and `b`, and returns the outputs specified in the truth table.

You can do this using traditional Python logic. **Or**, using a combination of the other gates you have learned about so far, you can make this in one line!

Hint

`OR_gate()` returns 1 if either `a` or `b` is 1.

Just like with the other gates, push yourself to use the previous gates in creating your `OR_gate()`!

One way to do this would be:

```
NAND(NAND(a, a), NAND(b, b))
```

Copy to Clipboard

Can you see why?

script.py

```
from nand import NAND_gate
from not_gate import NOT_gate
from and_gate import AND_gate
```

```
def OR_gate(a, b):
    return NAND_gate(NAND_gate(a, a), NAND_gate(b,b))
```

TEST CASES

```
print("A: 0, B: 0 | Output: {}".format(OR_gate(0, 0)))
```

```
print("A: 0, B: 1 | Output: {}".format(OR_gate(0, 1)))
```

```
print("A: 1, B: 0 | Output: {}".format(OR_gate(1, 0)))
```

```
print("A: 1, B: 1 | Output: {}".format(OR_gate(1, 1)))
```