

XOR Gate

3 min

Now, we are going to create what's called an *XOR gate*, an exclusive or gate. This gate receives two inputs, a and b, and only returns a 1 if one of the inputs is 1, but not if both of the inputs are 1.

To build your `XOR_gate()`, you should use any combination of the gates you've already made: `NAND_gate()`, `NOT_gate()`, `AND_gate()`, and `OR_gate()`.

Here's the truth table:

a	b	output
0	0	0
0	1	1
1	0	1
1	1	0

Instructions

1. Checkpoint 1 Passed

1.

Define `XOR_gate()` which takes two inputs, a and b, and returns the outputs specified in the truth table.

Hint

`XOR_gate()` returns 1 if either a or b is 1, but not if they're both 1.

Push yourself to use the previous gates in creating your `XOR_gate()`!

One way to do this would be:

```
AND(NAND(a, b), OR(a, b))
```

Copy to Clipboard

Can you see why?

script.py

```
from nand import NAND_gate
from not_gate import NOT_gate
from and_gate import AND_gate
from or_gate import OR_gate
```

```
# TEST CASES
```

```
def XOR_gate(a, b):
    return AND_gate(NAND_gate(a, b), OR_gate(a, b))
```

```
print("A: 0, B: 0 | Output: {}".format(XOR_gate(0, 0)))  
print("A: 0, B: 1 | Output: {}".format(XOR_gate(0, 1)))  
print("A: 1, B: 0 | Output: {}".format(XOR_gate(1, 0)))  
print("A: 1, B: 1 | Output: {}".format(XOR_gate(1, 1)))
```